

# Class 12 Physics - Current Electricity

JEE track | Short Notes + 5 CBSE-based questions + 5 JEE Main PYQ-based questions with solutions

Prepared by: Lakshya Institute Academic Desk	Focus: JEE + CBSE alignment
Format: Quick revision + solved practice	Chapter scope: Class 12 Physics

## 1. Quick Short Notes

- Current  $I = nqAv_d e$ , where  $n$  is free electron density,  $A$  is area,  $v_d$  is drift speed and  $e$  is electronic charge.
- Ohm's law:  $V = IR$  for ohmic conductors at constant temperature.
- Resistance of a wire:  $R = \rho l/A$ . Resistivity  $\rho$  is a material property and its SI unit is ohm-m.
- Current density  $J = I/A$  and  $J = \sigma E$ , where  $\sigma = 1/\rho$ .
- In series, resistances add:  $R_s = R_1 + R_2 + \dots$ ; in parallel,  $1/R_p = \sum(1/R_i)$ .
- Cell current:  $I = E/(R + r)$ , where  $E$  is emf,  $R$  is external resistance and  $r$  is internal resistance.
- Terminal voltage of a discharging cell:  $V = E - Ir$ .
- Kirchhoff's junction law is based on conservation of charge; loop law is based on conservation of energy.
- Potentiometer is a null-deflection device used to compare emf and measure internal resistance accurately.
- Board tip: write the reason while applying Kirchhoff laws and always show unit of resistivity and emf.

## 2. CBSE-based Board Practice

**Q1. A resistor of 5 ohm is connected across 10 V. Find the current through it.**

Solution: Using Ohm's law,  $I = V/R = 10/5 = 2$  A.

**Q2. A wire has resistance 4 ohm, length 2 m and cross-sectional area  $0.5 \text{ mm}^2$ . Calculate its resistivity.**

Solution:  $\rho = RA/l = 4 \times (0.5 \times 10^{-6})/2 = 1.0 \times 10^{-6}$  ohm-m.

**Q3. Two resistors 2 ohm and 3 ohm are connected in series across 10 V. Find current in the circuit and voltage across each resistor.**

Solution:  $R_{\text{total}} = 2 + 3 = 5$  ohm. Current  $I = 10/5 = 2$  A. Voltage drops:  $V_1 = 2 \times 2 = 4$  V,  $V_2 = 2 \times 3 = 6$  V.

**Q4. A cell of emf 2 V and internal resistance 0.5 ohm is connected to an external resistance of 3.5 ohm. Find the current and terminal voltage.**

Solution:  $I = E/(R + r) = 2/(3.5 + 0.5) = 0.5$  A. Terminal voltage  $V = E - Ir = 2 - 0.5 \times 0.5 = 1.75$  V.

**Q5. State the principle of a potentiometer. Why is it preferred over a voltmeter for measuring emf?**

Solution: Principle: the potential drop across a uniform wire is proportional to its length when a steady current flows through it. It is preferred because it works on null method and draws no current from the cell under test.

### 3. JEE Main PYQ-based Practice

**Q1. Two resistors 6 ohm and 3 ohm are connected in parallel across 12 V. Find the total current drawn from the battery.**

Solution:  $R_{eq} = (6 \times 3)/(6 + 3) = 2 \text{ ohm}$ . Total current  $I = 12/2 = 6 \text{ A}$ .

**Q2. In a metre bridge, balance point is obtained at 40 cm from the left end. If the left gap contains 2 ohm resistance, find the unknown resistance in the right gap.**

Solution: At balance,  $P/Q = l_1/l_2 = 40/60 = 2/3$ . With  $P = 2 \text{ ohm}$ ,  $2/Q = 2/3$ , so  $Q = 3 \text{ ohm}$ .

**Q3. The balancing lengths for two cells in a potentiometer are 300 cm and 250 cm. Find the ratio of their emfs.**

Solution: For a potentiometer, emf is proportional to balancing length. Therefore  $E_1/E_2 = 300/250 = 6/5$ .

**Q4. A cell of emf 12 V and internal resistance 2 ohm is connected to an external resistance. For what external resistance is the power delivered maximum? Also find the maximum power.**

Solution: Maximum power transfer occurs when external resistance  $R =$  internal resistance  $r = 2 \text{ ohm}$ .  $P_{max} = E^2/(4r) = 144/8 = 18 \text{ W}$ .

**Q5. Find the drift speed of electrons in a copper wire carrying 3.2 A current. Take  $n = 8 \times 10^{28} \text{ per m}^3$ , area =  $1 \times 10^{-6} \text{ m}^2$  and  $e = 1.6 \times 10^{-19} \text{ C}$ .**

Solution:  $v_d = I/(nAe) = 3.2 / (8 \times 10^{28} \times 1 \times 10^{-6} \times 1.6 \times 10^{-19}) = 2.5 \times 10^{-4} \text{ m/s}$ .

Practice tip: First revise the short notes, then attempt CBSE board questions in written format, and finally solve the exam-specific section in timed mode.