

Class 12 Physics - Current Electricity

NEET track | Short Notes + 5 CBSE-based questions + 5 NEET PYQ-based questions with solutions

Prepared by: Lakshya Institute Academic Desk	Focus: NEET + CBSE alignment
Format: Quick revision + solved practice	Chapter scope: Class 12 Physics

1. Quick Short Notes

- Current $I = nqAv_d e$, where n is free electron density, A is area, v_d is drift speed and e is electronic charge.
- Ohm's law: $V = IR$ for ohmic conductors at constant temperature.
- Resistance of a wire: $R = \rho l/A$. Resistivity ρ is a material property and its SI unit is ohm-m.
- Current density $J = I/A$ and $J = \sigma E$, where $\sigma = 1/\rho$.
- In series, resistances add: $R_s = R_1 + R_2 + \dots$; in parallel, $1/R_p = \sum(1/R_i)$.
- Cell current: $I = E/(R + r)$, where E is emf, R is external resistance and r is internal resistance.
- Terminal voltage of a discharging cell: $V = E - Ir$.
- Kirchhoff's junction law is based on conservation of charge; loop law is based on conservation of energy.
- Potentiometer is a null-deflection device used to compare emf and measure internal resistance accurately.
- Board tip: write the reason while applying Kirchhoff laws and always show unit of resistivity and emf.

2. CBSE-based Board Practice

Q1. A resistor of 5 ohm is connected across 10 V. Find the current through it.

Solution: Using Ohm's law, $I = V/R = 10/5 = 2$ A.

Q2. A wire has resistance 4 ohm, length 2 m and cross-sectional area 0.5 mm^2 . Calculate its resistivity.

Solution: $\rho = RA/l = 4 \times (0.5 \times 10^{-6})/2 = 1.0 \times 10^{-6}$ ohm-m.

Q3. Two resistors 2 ohm and 3 ohm are connected in series across 10 V. Find current in the circuit and voltage across each resistor.

Solution: $R_{\text{total}} = 2 + 3 = 5$ ohm. Current $I = 10/5 = 2$ A. Voltage drops: $V_1 = 2 \times 2 = 4$ V, $V_2 = 2 \times 3 = 6$ V.

Q4. A cell of emf 2 V and internal resistance 0.5 ohm is connected to an external resistance of 3.5 ohm. Find the current and terminal voltage.

Solution: $I = E/(R + r) = 2/(3.5 + 0.5) = 0.5$ A. Terminal voltage $V = E - Ir = 2 - 0.5 \times 0.5 = 1.75$ V.

Q5. State the principle of a potentiometer. Why is it preferred over a voltmeter for measuring emf?

Solution: Principle: the potential drop across a uniform wire is proportional to its length when a steady current flows through it. It is preferred because it works on null method and draws no current from the cell under test.

3. NEET PYQ-based Practice

Q1. State the SI unit of resistivity.

Solution: The SI unit of resistivity is ohm-metre (ohm-m).

Q2. Calculate the equivalent resistance of 2 ohm and 3 ohm connected in parallel.

Solution: $R_{eq} = (2 \times 3)/(2 + 3) = 6/5 = 1.2 \text{ ohm}$.

Q3. What happens to the resistance of a metallic conductor with increase in temperature?

Solution: For metals, resistance increases with increase in temperature because lattice vibrations increase and electron flow faces more opposition.

Q4. Kirchhoff's junction law is a consequence of which conservation principle?

Solution: It follows from conservation of charge.

Q5. A cell has emf 1.5 V and internal resistance 0.5 ohm. Find the short-circuit current.

Solution: For short circuit, external resistance is zero. $I = E/r = 1.5/0.5 = 3 \text{ A}$.

Practice tip: First revise the short notes, then attempt CBSE board questions in written format, and finally solve the exam-specific section in timed mode.